



Stamford University Bangladesh

Department of Computer Science and Engineering

Midterm Examination

Trimester: Summer 2022

Course Code: EEE 193

Course Title: Electrical Circuits & Devices

Batch # CSE 79(A+B)



Time: 3.00 Hours

Full marks: 30

All questions are compulsory.

Figures in the right margin indicate marks

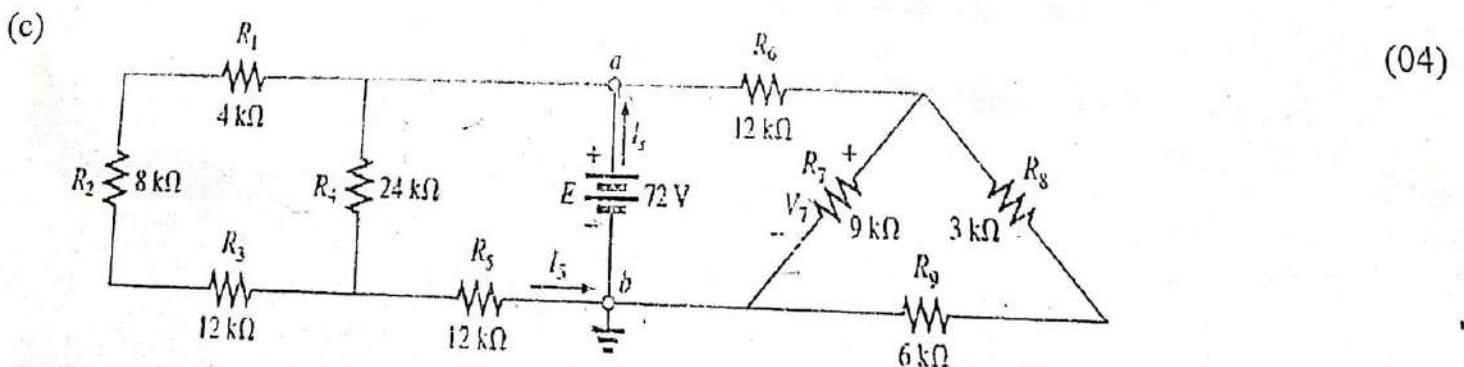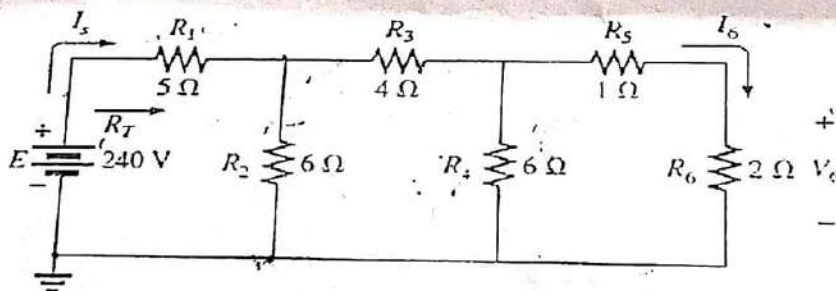
1. (a) Briefly explain Delta to Wye conversion and Wye to Delta conversion. (03)
- (b) If a $1\text{ k}\Omega$ and a $2\text{ k}\Omega$ resistor are parallel-connected across a 12 V supply, how much current is received by the $2\text{ k}\Omega$ resistor? (03)
- (c) According to electrical conductivity, how many types of materials are there and what are they? Describe in brief. (02)
- (d) Frequency is 50 Hz . What does it mean? (02)
2. (a) What is the value of a six-band resistor, which has band color Green, Blue, Black, Orange, Violet, and Brown? (02)
- (b) Determine unknown resistance, voltage and currents. (04)



Calculate the indicated currents and voltages.

3. (a)

(06)

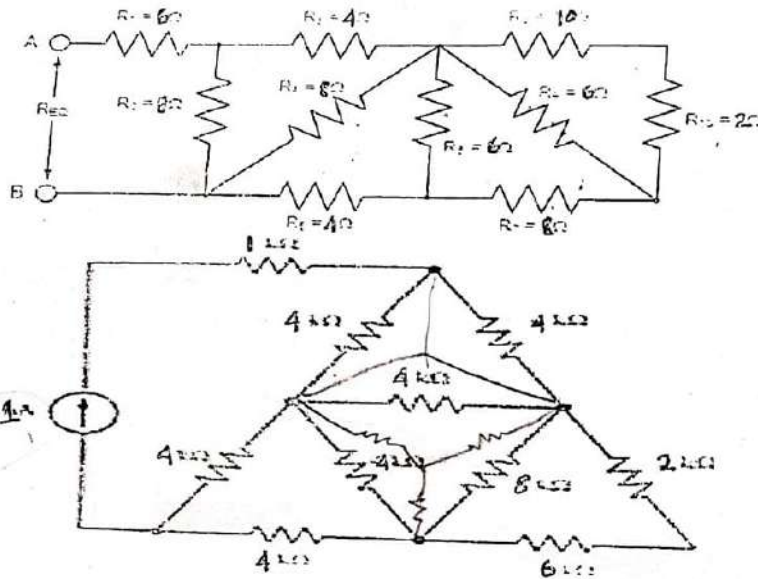

Determine the equivalent resistance of the following circuits.

- (b) The parallel combination of a 470Ω resistor and a $1.2k\Omega$ resistor is in series with the parallel combination of three $3k\Omega$ resistors. A $200V$ source is connected across the circuit. The resistor with the most current has a value of,...

(04)

$$I \times \frac{8}{2} =$$

